

ICS 2018 Problem Sheet #8

Problem 8.1: full adder using different kinds of gates

(1+1+1+1 = 4 points)

A full adder digital circuit was introduced in class. It is defined by the following two boolean functions:

$$\begin{aligned} S &= A \dot{\vee} B \dot{\vee} C_{in} \\ C_{out} &= (A \wedge B) \vee (C_{in} \wedge (A \dot{\vee} B)) \end{aligned}$$

- Write both functions as a disjunction of product terms.
- Write both functions as a conjunction of sum terms.
- Write both functions using only not (\neg) and not-and (\uparrow) operations.
- In a digital circuit, we can easily reuse common terms. Draw a small digital circuit implementing S and C_{out} using NAND gates only.

Problem 8.2: ripple carry adder and carry lookahead adder (haskell)

(1+1+2+2 = 6 points)

Your task is to implement a ripple carry adder and a carry lookahead adder. Binary numbers will be represented as a list of `Bool` values. We break things into small steps:

- Implement a function `bin m n` that converts the non-negative integer number `n` into a list of `Bools`. The list returned will have the length `m`.

```
ghci> bin 4 5
[False, True, False, True]
ghci> bin 8 42
[False, False, True, False, True, False, True, False]
```

- Implement a function `dec x` that converts a list of `Bool` values into the corresponding non-negative integer number.

```
ghci> dec [False, True, False, True]
5
ghci> dec [False, False, True, False, True, False, True, False]
42
```

- Implement the functions `faC` and `faS` that receive two input boolean values and a carry boolean value and calculate the carry (`faC`) and the sum (`faS`) of the full adder digital circuit. Use these two functions to implement `rcAdd`, a ripple carry adder. For simplicity, `rcAdd` is not returning the final carry bit.

```
ghci> rcAdd [False, True, False, True] [True, False, False, False]
[True, True, False, True]
```

Combining `rcAdd` with the other functions, you should be able to do computations like this:

```
ghci> dec (rcAdd (bin 4 5) (bin 4 8))
13
```

- Implement the functions `haC` and `haS` that receive two input boolean values and calculate the carry (`haC`) and the sum (`haS`) of the half adder digital circuit. Use these two functions to implement `claAdd`, a carry lookahead adder. It is sufficient to implement the carry calculator as a recursive function. For simplicity, `claAdd` is not returning the carry bit.

```
ghci> claAdd [False,True,False,True] [True,False,False,False]
[True,True,False,True]
ghci> dec (claAdd (bin 4 5) (bin 4 8))
13
```

Submit your Haskell code plus an explanation (in Haskell comments) as a plain text file.